 





Chapter 5: Logical Effort

Outline

- ☐ Logical Effort
- ☐ Delay in a Logic Gate
- ☐ Multistage Logic Networks
- ☐ Choosing the Best Number of Stages
- ☐ Example
- ☐ Summary


Introduction

- ❑ Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- ❑ Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

 

 Example

- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.




- ❑ Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

Delay in a Logic Gate

- ❑ Express delays in process-independent unit $d = \frac{d_{abs}}{\tau}$
 - ❑ Delay has two components: $d = f + p$
 - ❑ f : effort delay = gh (a.k.a. stage effort)
 - Again has two components
 - ❑ g : logical effort
 - Measures relative ability of gate to deliver current
 - $g \equiv 1$ for inverter
 - ❑ h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
 - ❑ p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance
- $\tau = 3RC$
 $\approx 3 \text{ ps in } 65 \text{ nm process}$
 $60 \text{ ps in } 0.6 \mu\text{m process}$


Delay Plots

$$d = f + p$$
$$= gh + p$$

 


Computing Logical Effort

 
- ❑ DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- ❑ Measure from delay vs. fanout plots
- ❑ Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	


Catalog of Gates

- ❑ Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$


Parasitic Delay: $p =$

Stage Delay: $d =$

Frequency: $f_{\text{osc}} =$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$


Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort* $G = \prod g_i$

❑ *Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 ❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$



Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort* $G = \prod g_i$

❑ *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$

❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$

❑ Can we write $F = GH$?

Paths that Branch

❑ No! Consider paths that branch:

G =


H =

GH =

h_1 =

h_2 =

F =

 

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

Multistage Delays

- ❑ Path Effort Delay $D_F = \sum f_i$
- ❑ Path Parasitic Delay $P = \sum p_i$
- ❑ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is



- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



Example: 3-stage path

 

Logical Effort $G =$

Electrical Effort $H =$

Branching Effort $B =$

Path Effort $F =$

Best Stage Effort $\hat{f} =$

Parasitic Delay $P =$


Delay $D =$

Example: 3-stage path

- Work backward for sizes

$y =$


$x =$

 

Best Number of Stages

- ❑ How many stages should a path use?
 - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter


D =

 

Derivation

- Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

Best Stage Effort

- ❑ $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- ❑ Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- ❑ For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

 
- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

 Example, Revisited

- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- ❑ Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort: $H =$

Branching Effort: $B =$

- ❑ If we neglect logical effort (assume $G = 1$)

Path Effort: $F =$

Number of Stages: $N =$

- ❑ Try a -stage design

Gate Sizes & Delay

Logical Effort: $G =$


Path Effort: $F =$

Stage Effort: $\hat{f} =$

Path Delay: $D =$

Gate sizes: $z =$

$y =$

 

Comparison

- ❑ Compare many alternatives with a spreadsheet
- ❑ $D = N(76.8 G)^{1/N} + P$

Design	N	G	P	D
NOR4	1	3	4	234
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Limits of Logical Effort

- ❑ Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- ❑ Simplistic delay model
 - Neglects input rise time effects
- ❑ Interconnect
 - Iteration required in designs with wire
- ❑ Maximum speed only
 - Not minimum area/power for constrained delay

Summary

- ❑ Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- ❑ Provides language for discussing fast circuits
 - But requires practice to master

Practice 1

Consider the two designs of a 2-input AND gate shown in Figure 4.39. Give an intuitive argument about which will be faster. Back up your argument with a calculation of the path effort, delay, and input capacitances x and y to achieve this delay.

 


FIGURE 4.39 2-input AND gate

(a) should be faster than (b) because the NAND has the same parasitic delay but lower logical effort than the NOR. In each design, $H = 6$, $B = 1$, $P = 1 + 2 = 3$. For (a), $G = (4/3) * 1 = (4/3)$. $F = GBH = 8$. $f = 8^{1/2} = 2.8$. $D = 2f + P = 8.6 \tau$. $x = 6C * 1/f = 2.14C$. For (b), $G = 1 * (5/3)$. $F = GBH = 10$. $f = 10^{1/2} = 3.2$. $D = 2f + P = 9.3 \tau$. $x = 6C * (5/3) / f = 3.16C$.

Practice 2

Consider four designs of a 6-input AND gate shown in Figure 4.40. Develop an expression for the delay of each path if the path electrical effort is H . What design is fastest for $H = 1$? For $H = 5$? For $H = 20$? Explain your conclusions intuitively.

 


FIGURE 4.40 6-input AND gate

Practice 2

 



FIGURE 4.40 6-input AND gate

$D = N(GH)^{1/N} + P$. Compare in a spreadsheet. Design (b) is fastest for $H = 1$ or 5. Design (d) is fastest for $H = 20$ because it has a lower logical effort and more stages to drive the large path effort. (c) is always worse than (b) because it has greater logical effort, all else being equal.

Design	G	P	N	$D (H=1)$	$D (H=5)$	$D (H=20)$
(a)	$8/3 \approx 1$	$6 + 1$	2	10.3	14.3	21.6
(b)	$5/3 \approx 5/3$	$3 + 2$	2	8.3	12.5	19.9
(c)	$4/3 \approx 7/3$	$2 + 3$	2	8.5	12.9	20.8
(d)	$5/3 \approx 1 \approx 4/3 \approx 1$	$3 + 1 + 2 + 1$	4	11.8	14.3	17.3


Practice 3

 Tính delay của đường G1-G2-G3-G4-G5 trong mạch thực hiện cổng XOR-2 ngõ vào ở Hình 3, sử dụng logical effort. Đồng thời tính size của các P và N transistors để đạt delay này. Biết điện dung ngõ vào (input capacitance) của inverter G1 = 3 units, và điện dung tải (load capacitance) của cổng G5 = 25 units.



Review

 1. What are t_{pdr} , t_{pdf} , t_f , t_r , t_{cdr} , t_{cdf} ?
2. Calculate arrive time of the following circuit:



3. Explain the delay estimation of a fanout-of-1 inverter (slide 10)
4. Explain the t_{pdr} and t_{pdf} delay estimation of 3-input NAND driving h identical gates (slide 15).
5. Estimate delay for the gates: AOI21, OAI31
6. What is logical effort?
7. What is parasitic delay?
8. Estimate the delay of the following gate:

